

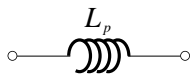
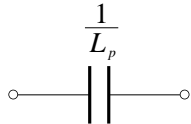
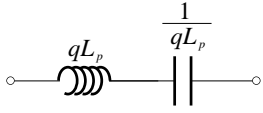
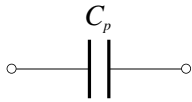
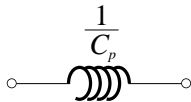
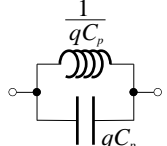

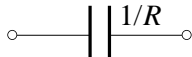
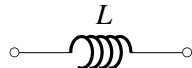
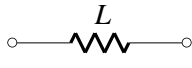


Passive and Active Analog Direct Filter Design

Step-by-step direct design of Butterworth filters for passive lowpass, highpass, and bandpass responses, and simulated element lowpass and highpass responses.



Design Steps

| | | | | | | |
|---|---|--|--|-------|--------|-------|
| Specification | | | | | | |
| Frequency Transformation | $\Omega_s = \frac{\omega_s}{\omega_p}$ | $\Omega_s = \frac{\omega_p}{\omega_s}$ | $\Omega_s = \frac{\omega_4 - \omega_3}{\omega_2 - \omega_1}$ $\omega_0^2 = \omega_1\omega_2 = \omega_3\omega_4$ | | | |
| Lowpass Prototype Specification | | | | | | |
| M | $M = \sqrt{\frac{10^{0.1K_s} - 1}{10^{0.1K_p} - 1}}$ | | | | | |
| Butterworth Order | $n = \frac{\ln M}{\ln \Omega_s}$ <p>Round up to an integer.</p> | | | | | |
| Minimum Inductance Doubly Terminated Lossless Ladder | | | | | | |
| Element values for a Butterworth response | n | C_1 | L_2 | C_3 | L_4 | C_5 |
| | 2 | 1.414 | 1.414 | | | |
| | 3 | 1.000 | 2.000 | 1.000 | | |
| | 4 | 0.7654 | 1.848 | 1.848 | 0.7654 | |
| | 5 | 0.618 | 1.618 | 2.000 | 1.618 | 0.618 |
| | n | L_1 | C_2 | L_3 | C_4 | L_5 |
| Minimum Capacitance Doubly Terminated Lossless Ladder | | | | | | |

D.2

| | | | |
|-------------------------------------|---|---|---|
| Ω_0 or q | $\Omega_{0p} = \frac{1}{(10^{0.1K_p} - 1)^{1/2n}} \quad \Omega_{0s} = \frac{\Omega_s}{(10^{0.1K_s} - 1)^{1/2n}}$ $\Omega_0 = \sqrt{\Omega_{0p}\Omega_{0s}}$ | | $q = \frac{\omega_0}{\omega_2 - \omega_1}$ |
| Element Transformation | Prototype (lowpass) elements | Highpass elements | Bandpass elements |
| |  |  |  |
| |  |  |  |
| Bruton Transformation (active only) |  | |  |
| |  | |  |
| |  | |  |
| Half-power or Centre Freq. | $\omega_0 = \omega_p \Omega_0$ | $\omega_0 = \frac{\omega_p}{\Omega_0}$ | $\omega_0 = \sqrt{\omega_1 \omega_2}$ |
| Scaling | $k_f = \omega_0, \text{ choose } k_m \text{ for proper element values.}$ | | |
| Gain | Fixed for passive filters, provide gain or attenuation to meet the K_0 specification for active filters. | | |

Simulated Element Circuits
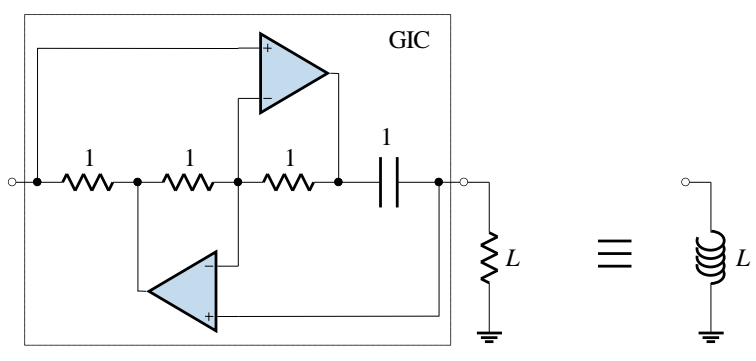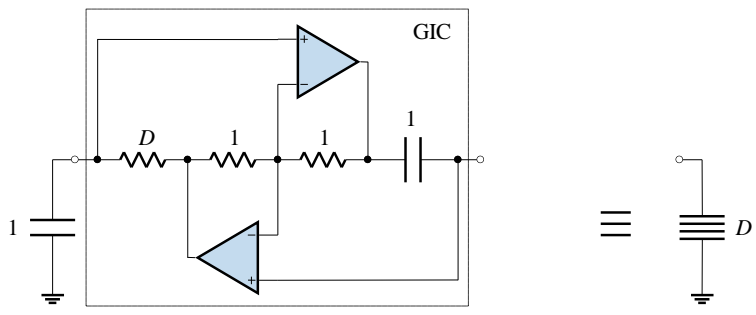
| | |
|----------|--|
| Inductor |  |
| FDNR |  |