

# Contents

## LECTURE 1A – ELECTROSTATICS

INTRODUCTION.....	1A.1
A BRIEF HISTORY OF ELECTROSTATICS .....	1A.2
VECTORS.....	1A.3
THE VECTOR DOT PRODUCT .....	1A.3
THE VECTOR CROSS PRODUCT .....	1A.5
AREA VECTORS .....	1A.6
COULOMB'S LAW .....	1A.7
THEORY .....	1A.7
THE ELECTRIC FIELD.....	1A.8
COMPUTER DEMO .....	1A.10
SUPERPOSITION .....	1A.10
POTENTIAL DIFFERENCE .....	1A.12
CURRENT DENSITY AND OHM'S LAW.....	1A.14
SURFACE INTEGRALS.....	1A.15
FLUX AND FLUX DENSITY .....	1A.16
GAUSS' LAW FOR ELECTROSTATICS .....	1A.17
SUMMARY .....	1A.18
PROBLEMS.....	1A.20

## LECTURE 1B – ELECTRODYNAMICS

REVISION.....	1B.1
COULOMB'S LAW .....	1B.1
POTENTIAL DIFFERENCE.....	1B.1
FLUX AND FLUX DENSITY .....	1B.1
GAUSS' LAW .....	1B.2
MAGNETS .....	1B.2
GAUSS' LAW FOR MAGNETOSTATICS .....	1B.3
LAW OF BIOT-SAVART .....	1B.4
MAGNETIC FIELD NEAR A LONG, THIN CONDUCTOR .....	1B.6
MAGNETIC SCALAR POTENTIAL .....	1B.7
AMPÈRE'S LAW .....	1B.7
RELUCTANCE, MAGNETOMOTIVE FORCE AND MAGNETIC CIRCUITS.....	1B.8
THE AXIAL FIELD OF A CURRENT LOOP .....	1B.10
THE AXIAL FIELD OF A SOLENOID.....	1B.11
THE LORENTZ FORCE .....	1B.13
ELECTROMOTIVE FORCE (EMF) .....	1B.14
FLUX LINKAGE.....	1B.16
FARADAY'S LAW .....	1B.17
INDUCTANCE.....	1B.18
SELF INDUCTANCE.....	1B.18
MUTUAL INDUCTANCE .....	1B.19
SUMMARY .....	1B.21
PROBLEMS.....	1B.23

**LECTURE 2A – CONDUCTORS AND INSULATORS**

THE BOHR ATOM.....	2A.1
THE ENERGY BARRIER .....	2A.4
BOUND AND FREE CHARGES.....	2A.5
ESCAPE FROM A SURFACE.....	2A.7
CONDUCTION.....	2A.8
DIELECTRICS .....	2A.10
THE ELECTRIC DIPOLE .....	2A.10
EFFECT OF BOUNDARIES.....	2A.11
POLARISATION.....	2A.14
FERROELECTRICS.....	2A.18
BREAKDOWN AT SHARP POINTS .....	2A.19
EXAMPLE – PARALLEL PLATE CAPACITOR .....	2A.21
EXAMPLE – AIR CAVITIES IN DIELECTRICS AND PARTIAL DISCHARGES.....	2A.24
EXAMPLE – VARIABLE PERMITTIVITY CAPACITOR .....	2A.27
EXAMPLE – ELECTROSTATIC GENERATOR (VAN DE GRAAFF GENERATOR) ..	2A.28
EXAMPLE – LORD KELVIN’S WATER DYNAMO.....	2A.29
SUMMARY .....	2A.30

**LECTURE 2B – MAGNETISM**

MAGNETIC DIPOLE MOMENT.....	2B.1
MAGNETISATION .....	2B.2
DIAMAGNETISM.....	2B.4
PARAMAGNETISM .....	2B.6
FERROMAGNETISM .....	2B.6
THE B-H CHARACTERISTIC (HYSTERESIS).....	2B.7
MINOR LOOPS .....	2B.10
THE NORMAL MAGNETIZATION CHARACTERISTIC .....	2B.11
SUMMARY .....	2B.12

**LECTURE 3A – SEMICONDUCTORS**

SEMICONDUCTOR STRUCTURE.....	3A.1
P-TYPE SEMICONDUCTOR.....	3A.3
N-TYPE SEMICONDUCTOR .....	3A.4
THE P-N JUNCTION.....	3A.5
REVERSE BIAS .....	3A.8
FORWARD BIAS.....	3A.9
JUNCTION CAPACITANCE .....	3A.9
THE P-N JUNCTION CHARACTERISTIC (DIODE $V$ - $I$ CHARACTERISTIC).....	3A.10
FORWARD BIAS.....	3A.11
REVERSE BIAS .....	3A.11
BREAKDOWN .....	3A.11
DIODE MODELS .....	3A.12
THE IDEAL DIODE MODEL .....	3A.12
THE CONSTANT VOLTAGE DROP MODEL.....	3A.15
THE PIECE-WISE LINEAR MODEL .....	3A.17
THE SMALL SIGNAL MODEL .....	3A.19
THE HALL-EFFECT DEVICE .....	3A.20
BREAKDOWN DIODES .....	3A.21

ZENER BREAKDOWN.....	3A.21
AVALANCHE BREAKDOWN.....	3A.21
THE PHOTODIODE.....	3A.21
THE LIGHT EMITTING DIODE (LED) .....	3A.21
THE SCHOTTKY DIODE.....	3A.22
THE VARACTOR DIODE .....	3A.22
SUMMARY .....	3A.23

### LECTURE 3B – FIELD MAPPING

THE METHOD OF CURVILINEAR SQUARES.....	3B.1
EXAMPLE – RECTANGULAR CONDUCTOR BETWEEN TWO EARTH PLANES .....	3B.8
EXAMPLE – CYLINDRICAL CONDUCTOR INSIDE METAL DUCT .....	3B.9
THE COAXIAL CABLE.....	3B.10
THE TWO CONDUCTOR TRANSMISSION LINE .....	3B.12
SUMMARY .....	3B.15

### LECTURE 4A – DIODE CIRCUITS

THE PEAK DETECTOR.....	4A.1
THE CLAMP CIRCUIT .....	4A.9
THE CLIPPING CIRCUIT.....	4A.12
GRAPHICAL ANALYSIS OF CLIPPING CIRCUIT .....	4A.13
SUMMARY .....	4A.16
PROBLEMS.....	4A.17

### LECTURE 4B – MAGNETIC CIRCUITS

THE MAGNETIC CIRCUIT .....	4B.1
MAGNETIC AND ELECTRIC EQUIVALENT CIRCUITS .....	4B.4
DC EXCITATION .....	4B.5
AC EXCITATION .....	4B.6
CHARACTERISTICS .....	4B.7
DETERMINING $\mathbf{F}$ GIVEN $\phi$ .....	4B.8
DETERMINING $\phi$ GIVEN $\mathbf{F}$ (LOAD LINE).....	4B.9
EQUIVALENT CIRCUIT OF A PERMANENT MAGNET.....	4B.11
EXAMPLE – DETERMINE $\mathbf{F}$ GIVEN $\phi$ .....	4B.14
EXAMPLE – PERMANENT MAGNET OPERATING POINT .....	4B.17
EXAMPLE – PERMANENT MAGNET MINIMUM VOLUME.....	4B.19
SUMMARY .....	4B.21
PROBLEMS.....	4B.22

### LECTURE 5A – GRAPHICAL ANALYSIS

THE STATIC CHARACTERISTIC .....	5A.1
THE DYNAMIC CHARACTERISTIC .....	5A.4
THE TRANSFER CHARACTERISTIC .....	5A.4
GRAPHICAL ANALYSIS .....	5A.5
THE SMALL SIGNAL DIODE MODEL .....	5A.6
THE LARGE SIGNAL DIODE MODEL .....	5A.7
SUMMARY .....	5A.9

**LECTURE 5B – FIELD ENERGY**

ENERGY STORED IN THE MAGNETIC FIELD.....	5B.1
ELECTRIC FIELD ENERGY .....	5B.7
TOTAL FIELD ENERGY .....	5B.7
HYSTERESIS LOSSES .....	5B.8
EDDY CURRENTS .....	5B.9
SUMMARY .....	5B.11
PROBLEMS .....	5B.12

**LECTURE 6A – RECTIFICATION**

CENTRE-TAPPED TRANSFORMER FWR CIRCUIT .....	6A.1
BRIDGE FWR CIRCUIT .....	6A.3
CAPACITOR FILTER.....	6A.4
ZENER REGULATOR .....	6A.6
SUMMARY .....	6A.7
PROBLEMS .....	6A.8

**LECTURE 6B – THE TRANSFORMER PRINCIPLE**

TRANSFORMER ELECTRIC AND MAGNETIC EQUIVALENT CIRCUITS.....	6B.1
STRAY CAPACITANCE .....	6B.8
SIGN CONVENTION .....	6B.8
SUMMARY .....	6B.9
PROBLEMS .....	6B.10

**MID-SEMESTER REVISION****LECTURE 7A - THE MOSFET**

THE MOSFET (N-CHANNEL).....	7A.1
-----------------------------	------

**LECTURE 7B – THE TRANSFORMER**

MAGNETISING BRANCH .....	7B.1
VOLTAGE, FLUX AND CURRENT WAVEFORMS.....	7B.3
PHASOR DIAGRAM.....	7B.6
LOSSES AND EFFICIENCY .....	7B.10
IRON LOSS .....	7B.10
COPPER LOSS .....	7B.10
EFFICIENCY .....	7B.10
MEASUREMENT OF TRANSFORMER PARAMETERS.....	7B.11
OPEN-CIRCUIT TEST .....	7B.11
SHORT-CIRCUIT TEST .....	7B.13
WINDING-RESISTANCE MEASUREMENTS .....	7B.16
CURRENT AND VOLTAGE EXCITATION .....	7B.17
CASE 1 - CURRENT EXCITATION .....	7B.17
CASE 2 - VOLTAGE EXCITATION .....	7B.17
3 <sup>RD</sup> HARMONICS .....	7B.18

**LECTURE 8A – THE MOSFET VOLTAGE AMPLIFIER**

SMALL SIGNAL EQUIVALENT CIRCUIT .....	8A.1
THE COMMON-SOURCE AMPLIFIER .....	8A.5
DC ANALYSIS.....	8A.5
DC DESIGN.....	8A.8
AC ANALYSIS.....	8A.9
AC DESIGN.....	8A.12
THE COMMON DRAIN (OR SOURCE FOLLOWER) AMPLIFIER.....	8A.12

**LECTURE 8B – THE FORCE EQUATION**

FORCE EQUATION OF SINGLY EXCITED ELECTROMECHANICAL TRANSDUCER ....	8B.1
ELECTRIC FIELD TRANSDUCER.....	8B.5
ELECTROSTATIC VOLTMETER .....	8B.6
PROBLEMS.....	8B.8

**LECTURE 9A – THE BIPOLAR JUNCTION TRANSISTOR**

PRINCIPLE OF THE BIPOLAR JUNCTION TRANSISTOR (BJT) .....	9A.1
INPUT AND OUTPUT CHARACTERISTICS.....	9A.3
BIASING CIRCUIT .....	9A.4
SMALL SIGNAL EQUIVALENT CIRCUIT .....	9A.7
COMMON EMITTER VOLTAGE AMPLIFIER .....	9A.8
THE EMITTER FOLLOWER.....	9A.9

**LECTURE 9B – THE MOVING COIL MACHINE**

GENERATOR PRINCIPLE .....	9B.1
ADVANTAGE OF AC GENERATION.....	9B.3
GENERATION OF SINUSOIDAL VOLTAGES .....	9B.3
ELECTRICAL EQUIVALENT CIRCUIT.....	9B.4
MOTOR (OR METER) PRINCIPLE .....	9B.4
MOVING COIL METER .....	9B.5

**LECTURE 10A - FREQUENCY RESPONSE**

THE AMPLIFIER BLOCK .....	10A.1
VOLTAGE AMPLIFIER .....	10A.2
CURRENT AMPLIFIER .....	10A.3
MAXIMUM POWER TRANSFER.....	10A.4
THE DECIBEL (dB) .....	10A.5
FREQUENCY RESPONSE OF CAPACITIVELY COUPLED CIRCUITS .....	10A.7
MID-FREQUENCIES .....	10A.8
CORNER FREQUENCY .....	10A.8
LOW FREQUENCIES.....	10A.9
GRAPHICAL ANALYSIS .....	10A.10
PROBLEMS.....	10A.12

**LECTURE 10B – BRIDGES AND MEASUREMENTS**

GENERAL BRIDGE EQUATIONS .....	10B.1
MEASUREMENT OF RESISTANCE .....	10B.2
MEASUREMENT OF INDUCTANCE .....	10B.8
MEASUREMENT OF CAPACITANCE .....	10B.10
AVERAGE AND RMS VALUES OF PERIODIC WAVEFORMS .....	10B.11
PROBLEMS .....	10B.14

**LECTURE 11A – THE OPERATIONAL AMPLIFIER**

THE EMITTER-COUPLED DIFFERENTIAL AMPLIFIER .....	11A.1
DC CONDITIONS .....	11A.2
AC CONDITIONS .....	11A.3
COMMON MODE.....	11A.4
DIFFERENTIAL MODE.....	11A.7
COMMON-MODE REJECTION RATIO .....	11A.9
THE OPERATIONAL AMPLIFIER .....	11A.10

**LECTURE 11B – METERS**

THE MOVING IRON METER .....	11B.1
ADVANTAGES .....	11B.2
DISADVANTAGES .....	11B.2
THE ELECTRODYNAMIC METER (WATTMETER) .....	11B.3
AMMETER .....	11B.4
VOLTMETER.....	11B.4
ELECTROMECHANICAL WATTMETER .....	11B.5
THE OHMMETER .....	11B.6
ELECTRONIC METERS .....	11B.8
THE ANALOG AC VOLTMETER.....	11B.8
THE DIFFERENTIAL VOLTMETER .....	11B.11
THE DIGITAL METER .....	11B.11
INTEGRATING ADC.....	11B.12
MICROPROCESSOR CONTROLLED.....	11B.13

**LECTURE 12A – OP-AMP CIRCUITS**

AN OP-AMP MODEL .....	12A.1
THE IDEAL OP-AMP.....	12A.2
THE INVERTING AMPLIFIER .....	12A.3
GAIN .....	12A.4
INPUT RESISTANCE .....	12A.4
OUTPUT RESISTANCE.....	12A.4
EFFECT OF FINITE OPEN-LOOP GAIN .....	12A.5
RESISTOR $R_4$ .....	12A.9
THE NONINVERTING AMPLIFIER .....	12A.11
THE VOLTAGE FOLLOWER.....	12A.12
AN ADDER CIRCUIT.....	12A.13
INTEGRATOR CIRCUITS .....	12A.14
A PRECISION HALF WAVE RECTIFIER.....	12A.16

**REVISION****ANSWERS**